

# Beta-Multiplier : A Step-by-Step Guide to Understanding


Dr. Anil Kumar Gundu




# A Systematic and Simplified View of Beta-Multiplier

- One way to bias the devices  $M_{n1}$  and  $M_{n2}$  is to push the same current to both devices
- How can this be done? Use a matched current mirror (pmos in this case) as it will make sure that  $M_{n1}$  and  $M_{n2}$  carries same current
- We have two options to push same current to the devices  $M_{n1}$  and  $M_{n2}$  (shown below left and right):
  - Which option works without any problem

Option-1

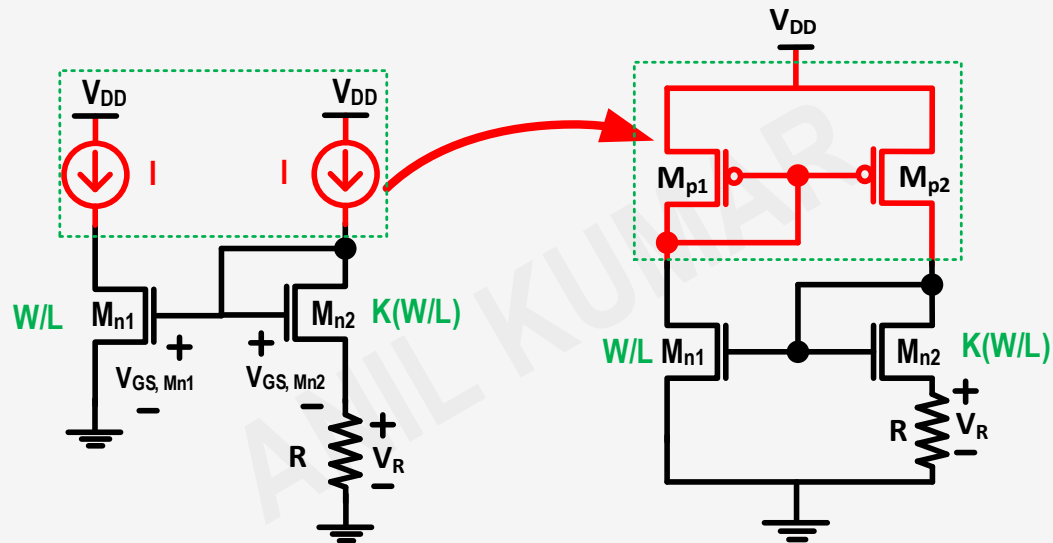


Option-2

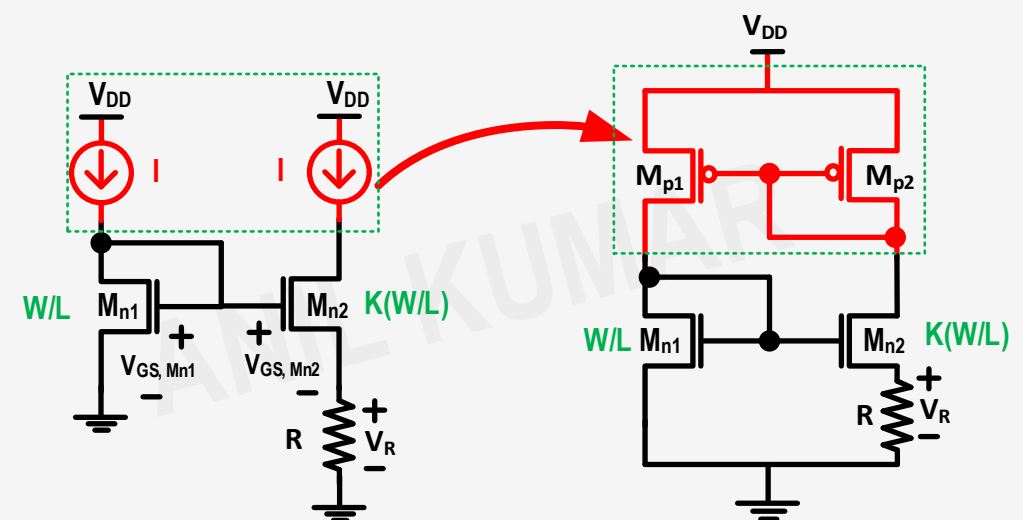
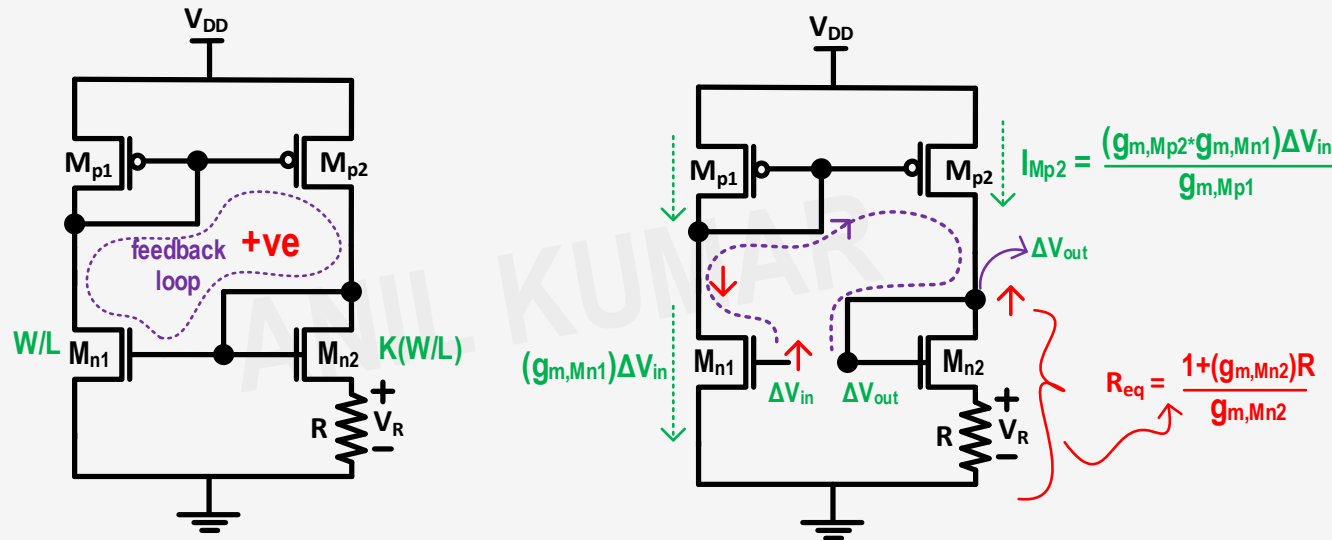
# A Systematic and Simplified View of Beta-Multiplier – Option 1

- It's a positive feedback loop. The loop gain is larger than 1.
- The loop gain and related analysis is shown below.
- The open loop gain in this case is strictly greater than 1 for any  $K > 1$



$$\Delta V_{out} = \frac{1 + (g_{m,Mn2})R}{g_{m,Mn2}} \frac{(g_{m,Mp2} * g_{m,Mn1}) \Delta V_{in}}{g_{m,Mp1}}$$

$$g_{m,Mn2} = \sqrt{K} * g_{m,Mn1}$$


perfectly matched current mirror yield,

$$\Delta V_{out} = \frac{[1 + (g_{m,Mn2})R] (g_{m,Mn1}) \Delta V_{in}}{g_{m,Mn2}}$$

$$\Delta V_{out} = \frac{[1 + (g_{m,Mn2})R] \Delta V_{in}}{\sqrt{K}}$$
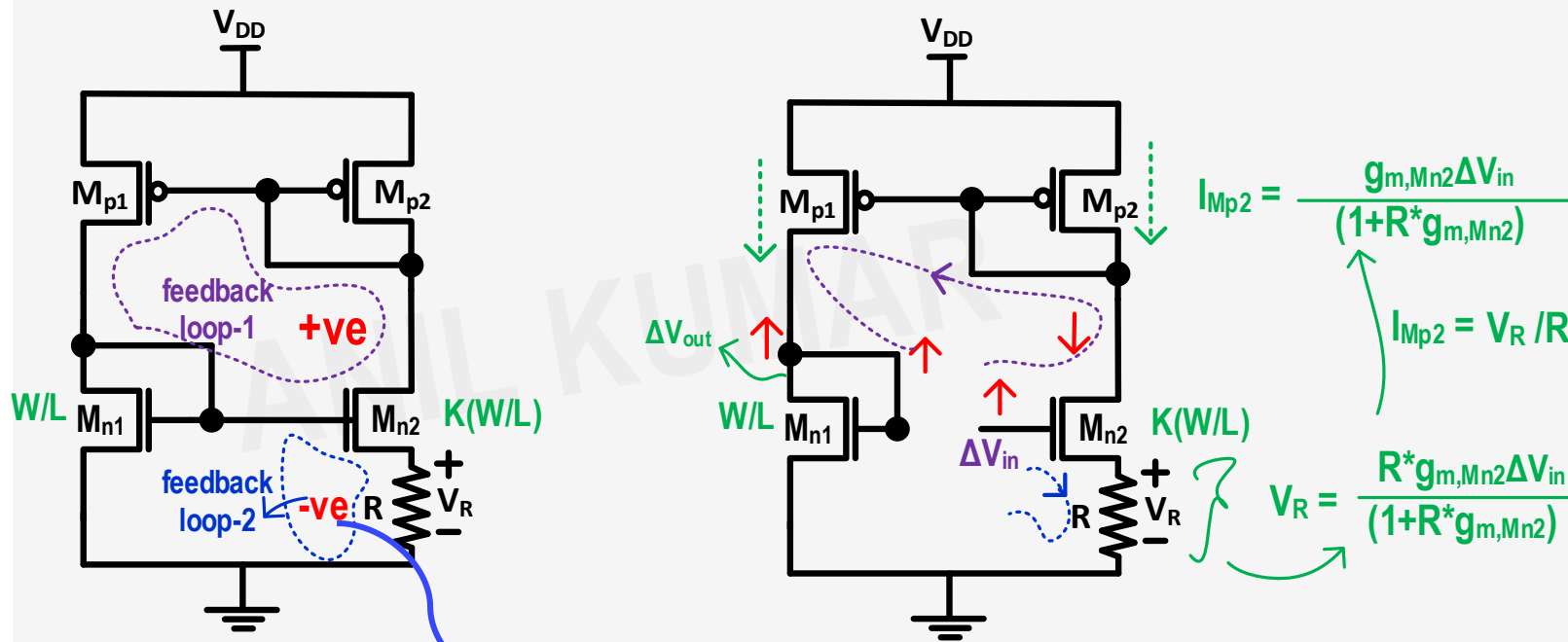
# A Systematic and Simplified View of Beta-Multiplier – Option 2

- It's a positive feedback loop. But the loop gain is smaller than 1.
- The loop gain and related analysis is shown below.
- The open loop gain in this case is strictly less than 1 for any  $K > 1$





$$\Delta V_{out} = \frac{g_{m,Mn2} \Delta V_{in}}{(1 + R^* g_{m,Mn2})} \frac{1}{g_{m,Mn1}}$$

$$\Delta V_{out} = \frac{\sqrt{K} \Delta V_{in}}{(1 + R^* g_{m,Mn2})}$$

This loop effectively helps in keeping loop gain less than 1

# Beta-Multiplier at a Glance

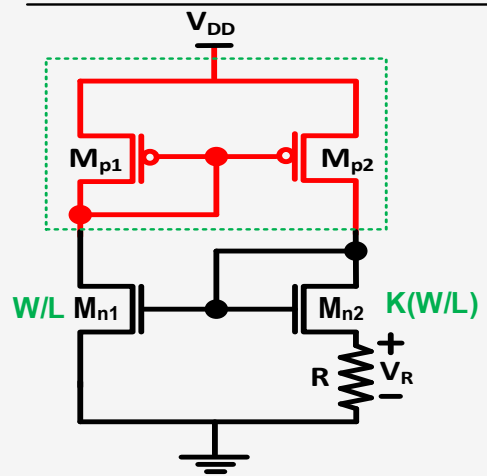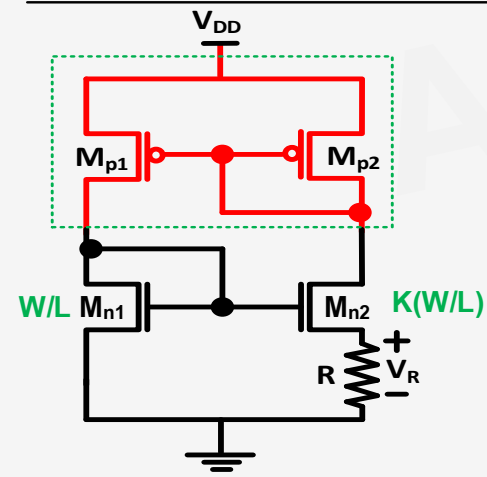	feedback	DC Loop Gain	stability	gm
	positive	$\Delta V_{out} = \frac{2\sqrt{K}-1}{\sqrt{K}} \Delta V_{in}$ <p>Loop gain is greater than 1</p> $> 1$	unstable	gm is not stabilized
	positive	$\Delta V_{out} = \frac{\sqrt{K}}{2\sqrt{K}-1} \Delta V_{in}$ <p>Loop gain is less than 1</p> $< 1$	stable	$g_{m,Mn1}R = \frac{2(\sqrt{K}-1)}{\sqrt{K}}$ <p>(constant)</p>