

The Beta-Multiplier: A Step-by-Step Guide to Understanding

Dr. Anil Kumar Gundu




Important Points / Notes for the technology file incorporation SKY130A

- Pick the symbols either of the paths :
- /usr/local/share/pdk/sky130A/libs.tech/xschem/sky130_fd_pr/
or
- /usr/local/share/pdk/sky130B/libs.tech/xschem/sky130_fd_pr/
- But make sure that library you are directing for the symbols you chose from above paths should be
.lib /usr/local/share/pdk/sky130A/libs.tech/ngspice/sky130.lib.spice tt
- tt means typical-typical corner (use appropriately the desired corner)

dc_sweep

 
```
.lib /usr/local/share/pdk/sky130A/libs.tech/ngspice/sky130.lib.spice tt
.dc VG 0 1.8 0.01
.save @XM1[gm]
.save I(vds)
.save @m.xm1.msky130_fd_pr__nfet_01v8_1vt[vth]
.save @m.xm1.msky130_fd_pr__nfet_01v8[cgg]
.save @m.xm1.msky130_fd_pr__nfet_01v8[ft]
.save all
.end
```




A Systematic and Simplified View of Beta-Multiplier

- One way to bias the devices M_{n1} and M_{n2} is to push the same current to both devices
- How can this be done? Use a matched current mirror (pmos in this case) as it will make sure that M_{n1} and M_{n2} carries same current
- We have two options to push same current to the devices M_{n1} and M_{n2} (shown below left and right):
 - Which option works without any problem

Option-1

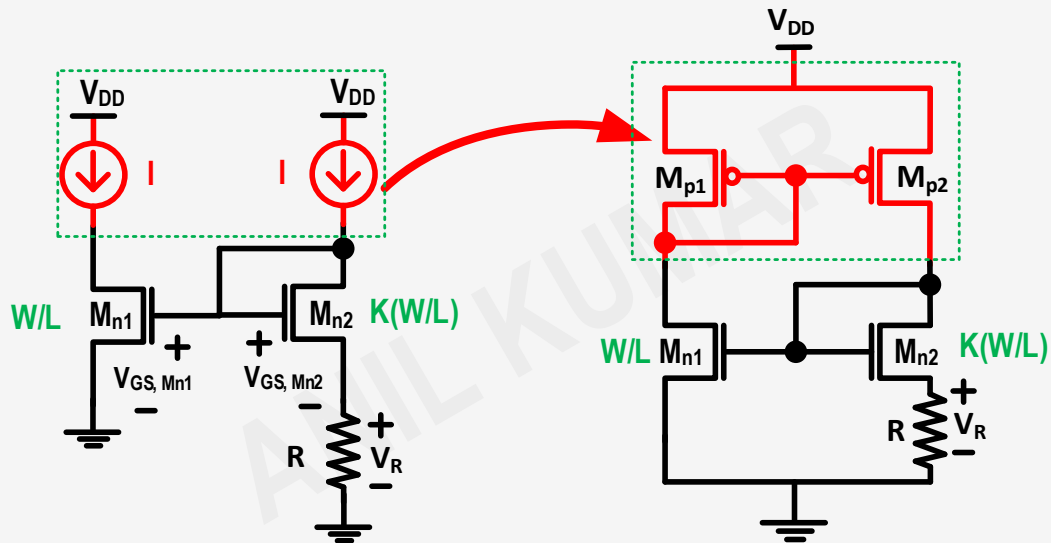


Option-2

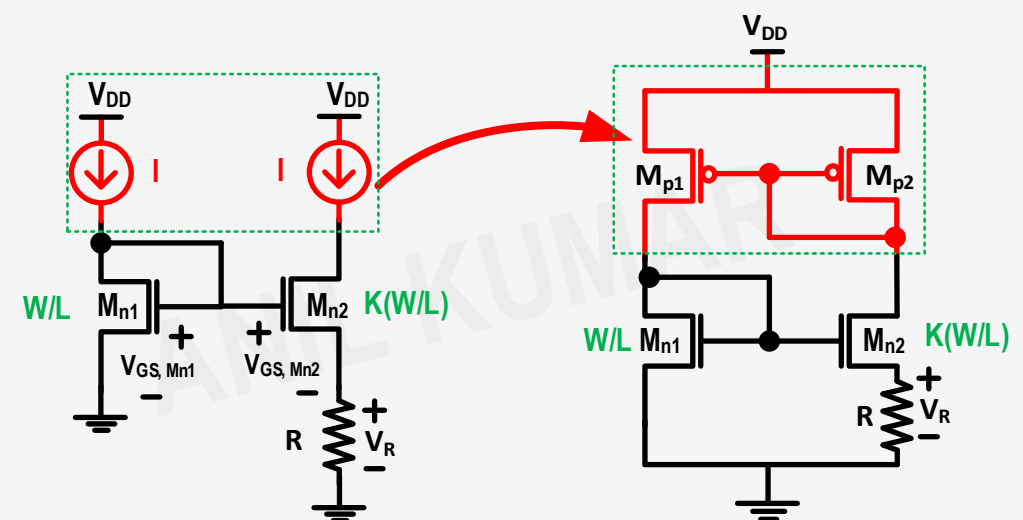

A Systematic and Simplified View of Beta-Multiplier – Option 1

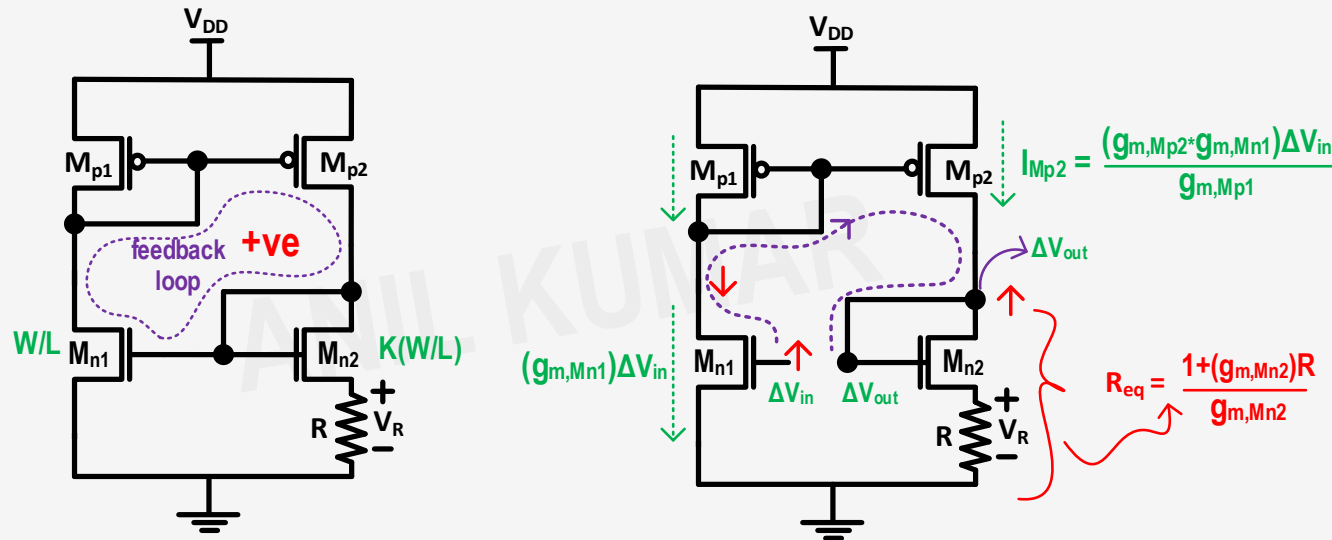- It's a positive feedback loop. The loop gain is larger than 1.
- The loop gain and related analysis is shown below.
- The open loop gain in this case is strictly greater than 1 for any $K > 1$



$$\Delta V_{out} = \frac{1+(g_{m,Mn2})R}{g_{m,Mn2}} \frac{(g_{m,Mp2} \cdot g_{m,Mn1}) \Delta V_{in}}{g_{m,Mp1}}$$

$$g_{m,Mn2} = \sqrt{K} \cdot g_{m,Mn1}$$


perfectly matched current mirror yield,

$$\Delta V_{out} = \frac{[1+(g_{m,Mn2})R](g_{m,Mn1}) \Delta V_{in}}{g_{m,Mn2}}$$

$$\Delta V_{out} = \frac{[1+(g_{m,Mn2})R] \Delta V_{in}}{\sqrt{K}}$$

A Systematic and Simplified View of Beta-Multiplier – Option 2

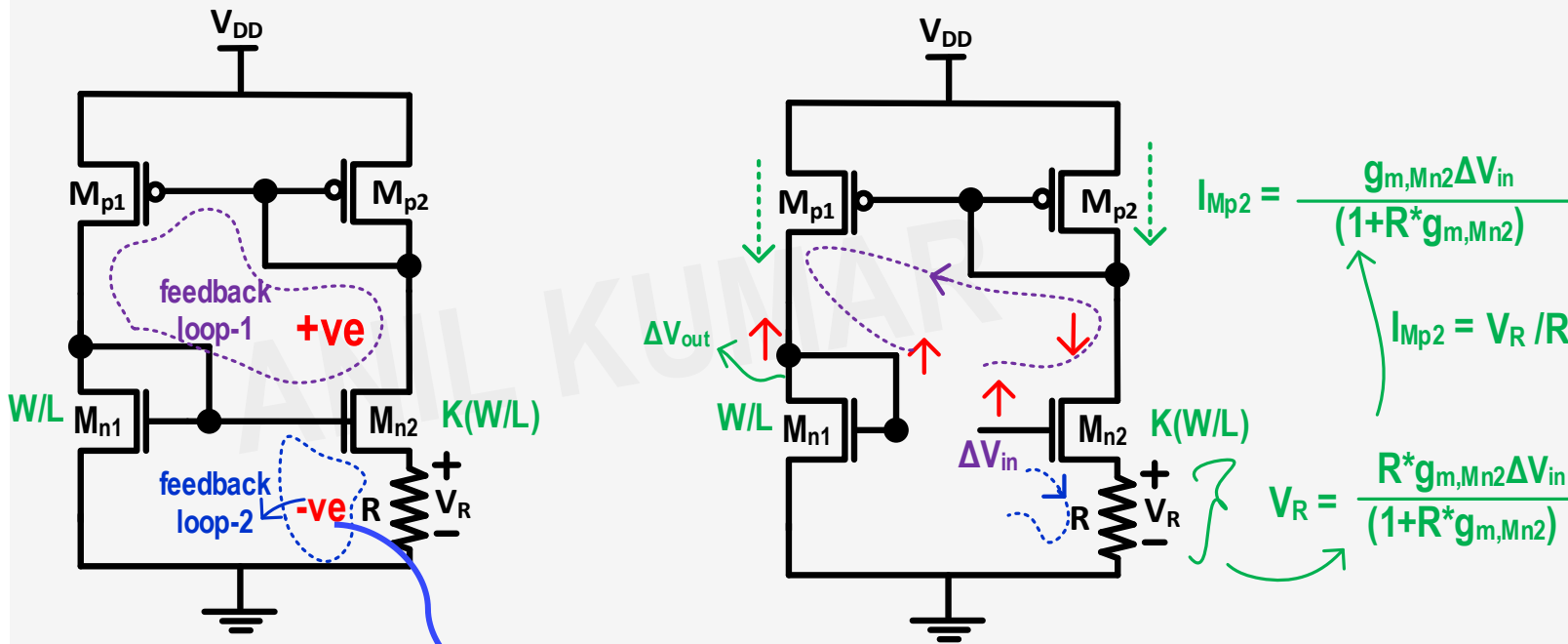- It's a positive feedback loop. But the loop gain is smaller than 1.
- The loop gain and related analysis is shown below.
- The open loop gain in this case is strictly less than 1 for any $K > 1$





This loop effectively helps in keeping loop gain less than 1

$$\Delta V_{out} = \frac{g_{m,Mn2} \Delta V_{in}}{(1 + R \cdot g_{m,Mn2})} \cdot \frac{1}{g_{m,Mn1}}$$




$$\Delta V_{out} = \frac{\sqrt{K} \Delta V_{in}}{(1 + R \cdot g_{m,Mn2})}$$

Beta-Multiplier at a Glance

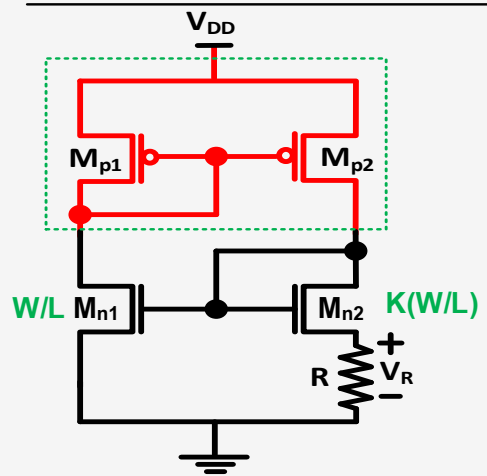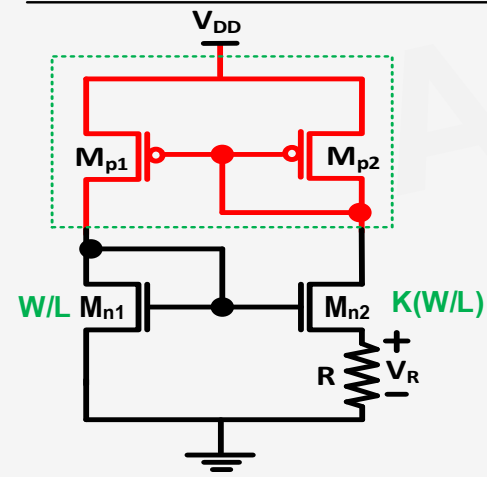	feedback	DC Loop Gain	stability	gm
	positive	$\Delta V_{out} = \frac{2\sqrt{K}-1}{\sqrt{K}} \Delta V_{in}$ <p>Loop gain is greater than 1</p> > 1	unstable	gm is not stabilized
	positive	$\Delta V_{out} = \frac{\sqrt{K}}{2\sqrt{K}-1} \Delta V_{in}$ <p>Loop gain is less than 1</p> < 1	stable	$g_{m,Mn1}R = \frac{2(\sqrt{K}-1)}{\sqrt{K}}$ <p>(constant)</p>

Gm Tracking: Off-Chip Resistor Impact



- Let us say, for a given sizing of the devices, transconductance (g_m) perfectly tracks the inverse of the off-chip resistor (R), meaning $g_m = 1/R$ and sets the operating point at 'A'.
- Here's how variations in the resistor R affect the operating point and transconductance:
- If the resistor R increases to $2R$:
 - Ideally, the current in device M_{n2} should halve and this current will be mirrored to M_{p1}
 - However, the operating point of M_{n1} shifts along the blue contour to 'C'.
 - This indicates that the actual g_m is higher than its expected value (which should be $1/(2R)$).
- Similarly, If the resistor R decreases to $R/2$. The operating point moves towards 'B'.
 - In this scenario, g_m decreases, or. the devices may even **move out of saturation**

   





Characterized using open-source skywater 130nm PDK

Gm Tracking: Off-Chip Resistor Impact

 
 
- If the off-chip resistor is increased or decreased, will this gm still be tracked accurately, if not how the error is going to behave.
- Let us say, for a given sizing of the devices, the gm is perfectly tracked and the $g_m = 1/R$ for the off-chip resistor of R. Now let's



Simulations (SKYWATER 130nm PDK)

    


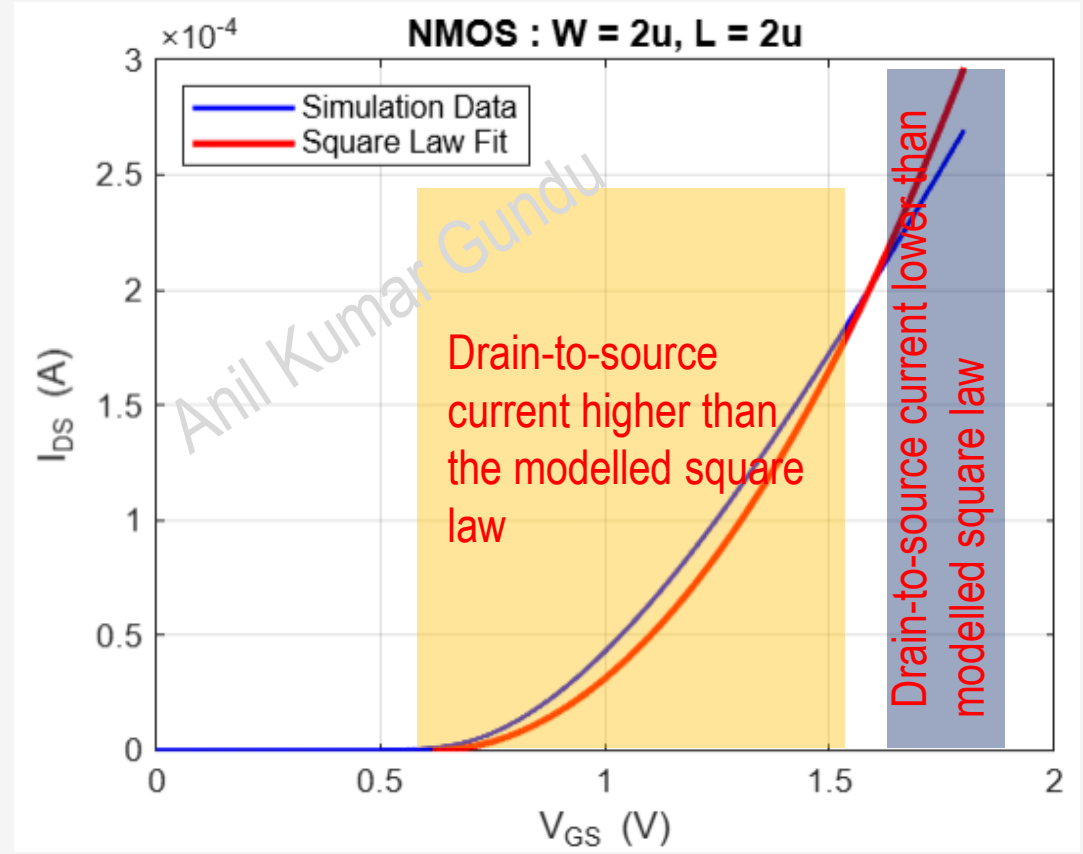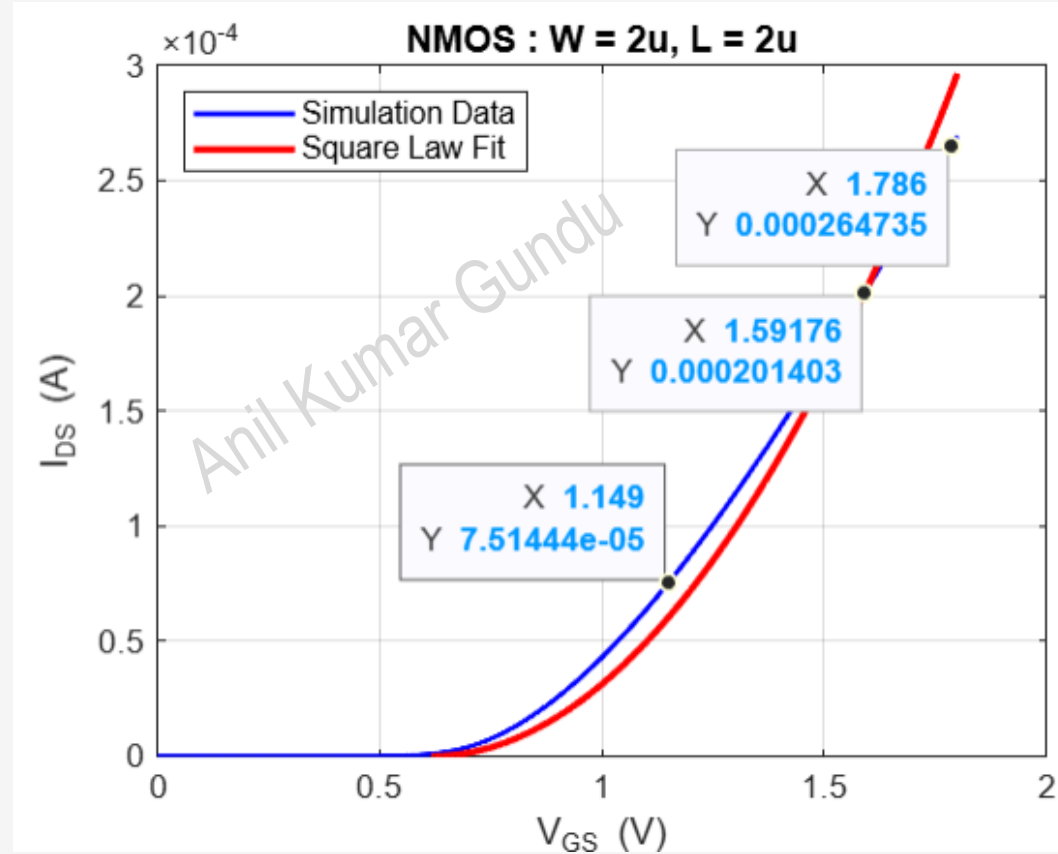NMOS: W/L is (2 μ m/1 μ m) and V_{DS} is 1.8V and V_{GS} is varied from 0V to 1.8V



Threshold Voltage (V_t) = 603.456 mV

 NMOS: W/L is (2 μ m/1 μ m): Transconductance plot and square law fit




Little deviation from square law model

Larger deviation from square law model

In this region, the transconductance matches the square-law behavior, indicating the device operates within the ideal square-law regime of the I-V characteristics.

NMOS Transconductance Characterization (V_{DS} is 1.8V and V_{GS} is varied from 0V to 1.8V)

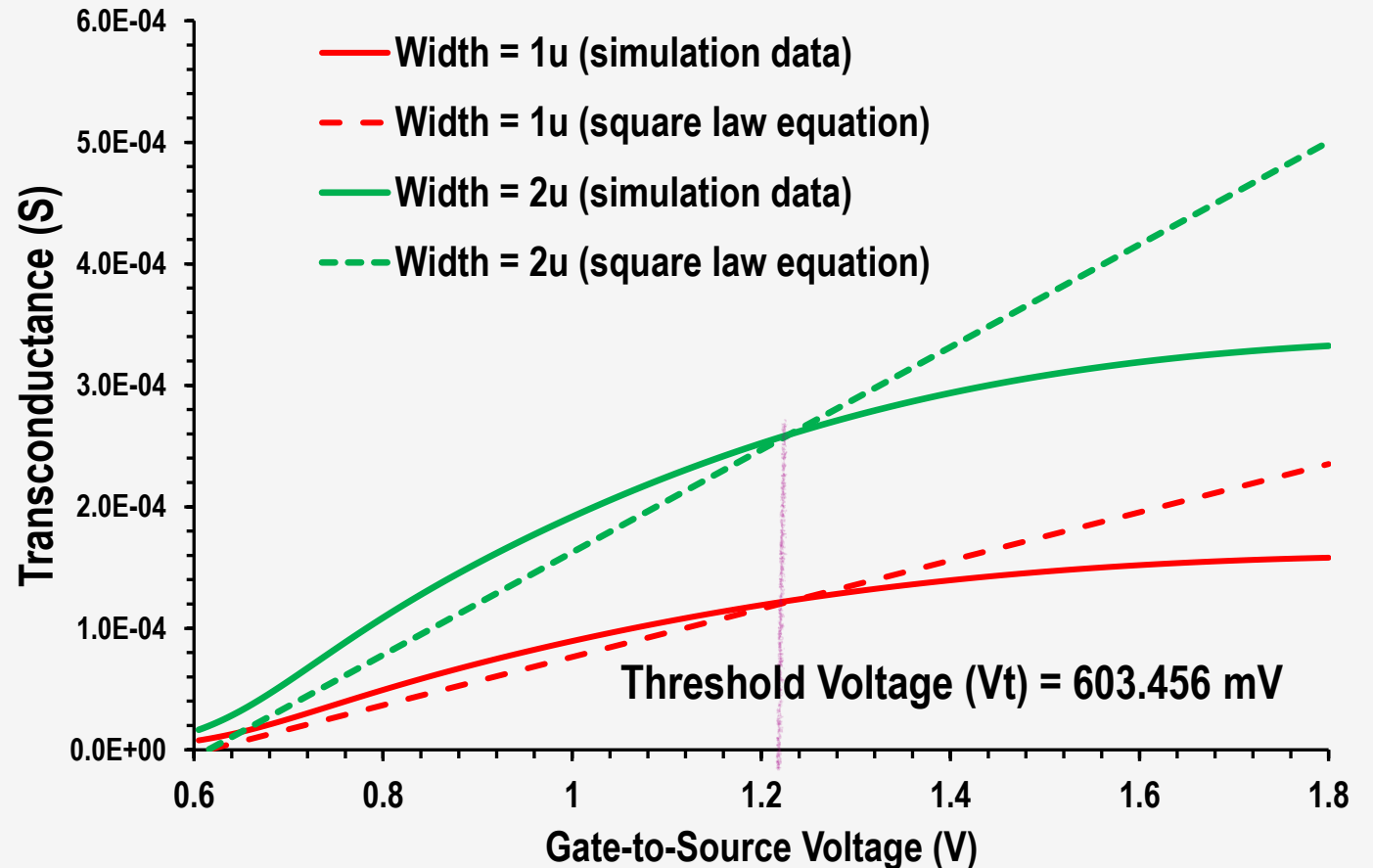
- When varying the current in a MOS device of a given size (from maximum to minimum or vice versa), the transconductance aligns with the ideal square law at a particular current value. The further the current moves from this point, the greater the error or deviation*



- We often approximate the I_{DS} - V_{GS} relationship with a square law, but in reality, the current scales with V_{GS} to an exponent typically ranging from 1 to 2. This non-ideal behavior means that relying on the simple square law equation will result in significant deviation in the calculated transconductance g_m .

NMOS Transconductance Characterization (V_{DS} is 1.8V and V_{GS} is varied from 0V to 1.8V)

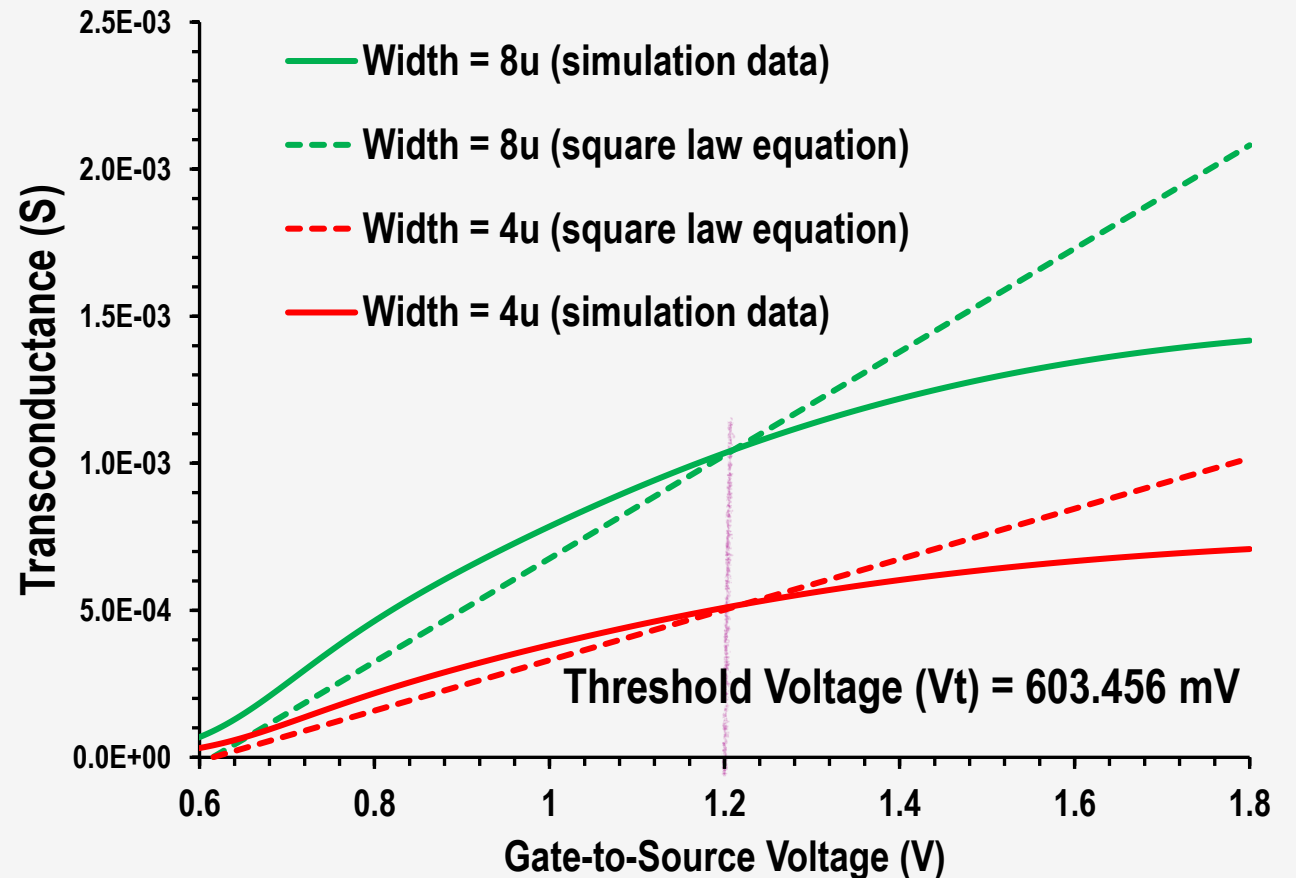- When varying the current in a MOS device of a given size (from maximum to minimum or vice versa), the transconductance aligns with the ideal square law at a particular current value. The further the current moves from this point, the greater the error or deviation



- We often approximate the I_{DS} - V_{GS} relationship with a square law, but in reality, the current scales with V_{GS} to an exponent typically ranging from 1 to 2. This non-ideal behavior means that relying on the simple square law equation will result in significant deviation in the calculated transconductance g_m .

Appendix

PMOS Critical Data : Threshold Voltage

- Threshold voltage of the nmos (130nm google SKY130A) devices are extracted at a nominal temperature of 27°C for the following devices (TT corner):
- Width = 1um and L = 0.15um

Device	Device	VDD (max)	Type	Threshold Voltage (mV)
pfet_01v8	PMOS	1.8	Nominal	510.3
pfet_01v8_hvt	PMOS	1.8	High V_t	660.9
pfet_01v8_lvt	PMOS	1.8	Low V_t	282.5
pfet_01v8_nf	PMOS	1.8	Nominal V_t (with fingers)	510.3
pfet_01v8_hvt_nf	PMOS	1.8	High V_t (L =0.35u with fingers)	775.6
pfet_01v8_lvt_nf	PMOS	1.8	Low V_t (with fingers)	282.5

- More details on the device voltages and their characteristics, refer <https://skywater-pdk.readthedocs.io/en/main/rules/device-details.html>

NMOS Critical Data: Threshold Voltage

- Threshold voltage of the nmos (130nm google SKY130A pdk) devices are extracted at a nominal temperature of 27°C for the following devices (TT corner):
- Width = 1um and L = 0.15um


Device	Device	VDD (max)	Type	Threshold Voltage (mV)
nfet_01v8	NMOS	1.8	Nominal	769.2
nfet_03v3_nvt	NMOS	1.8	Native V_t	0
nfet_01v8_lvt	NMOS	1.8	Low V_t	570.48
nfet_01v8_nf	NMOS	1.8	Nominal V_t (with fingers)	769.2
nfet_01v8_esd_nvt_nf	NMOS	1.8	Native V_t (with fingers)	686.5
nfet_01v8_lvt_nf	NMOS	1.8	Low V_t (with fingers)	570.48
Nfet_20v0_nf	NMOS	20	Zero V_t	0

- More details on the device voltages and their characteristics, refer <https://skywater-pdk.readthedocs.io/en/main/rules/device-details.html>

NMOS: Square Law Fitting (I_{ds} vs V_{gs})


- Channel length of the NMOS is varied for an NMOS with width of 4 μ m and then the square law equation is fitted.
- Approximately the V_{th} is chosen (approximately chosen) and checked the R^2 value.
- Device is forming mostly square law

Length (μ m)	K	R^2
0.5	0.000537	0.9967
1	0.000307	0.9975
1.5	0.000217	0.9983
2	0.000165	0.9985
2.5	0.000134	0.9986
3	0.000113	0.9986
3.5	9.71e-05	0.9986
4	8.53e-05	0.9987

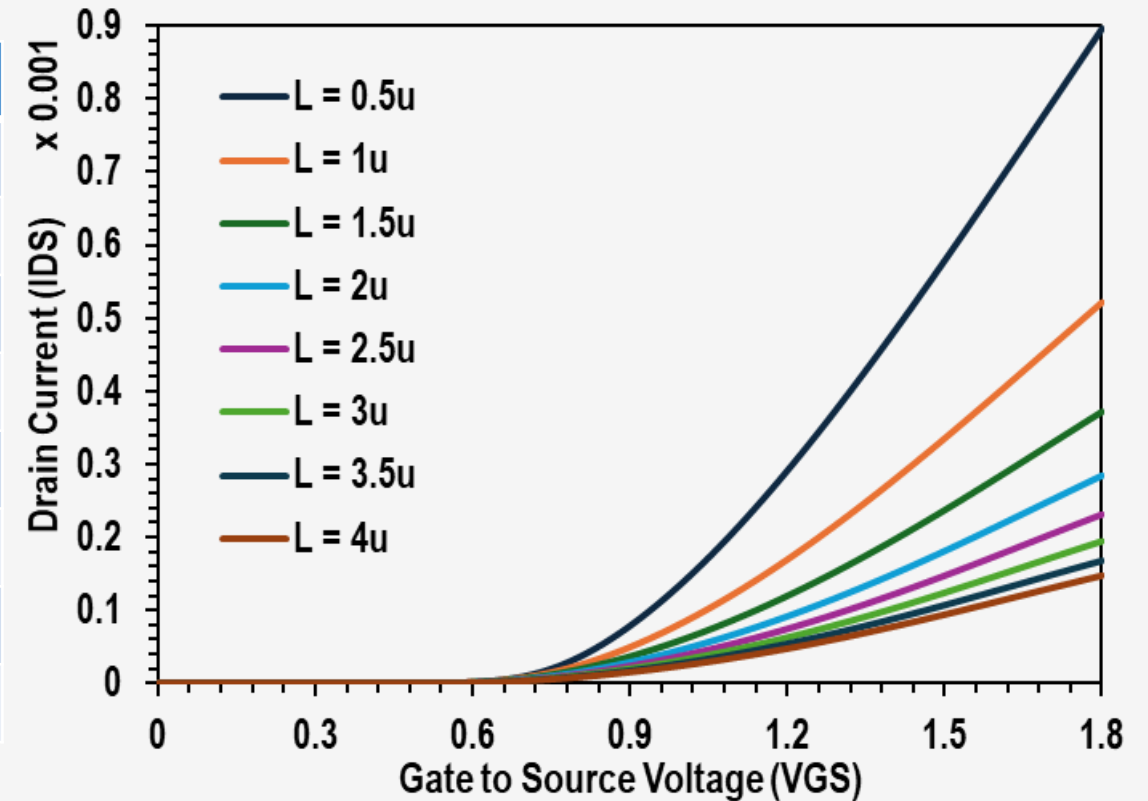


NMOS: W/L is (1 μ m/1 μ m) and V_{DS} is 1.8V and V_{GS} is varied from 0V to 1.8V

- Define an Operating Point: First, establish a specific operating point for the MOSFET by determining values for gate-to-source voltage (V_{GS}), drain current (I_{DS}), and drain-to-source voltage (V_{DS}).
- Differentiate I_{DS} with respect to V_{GS}: The transconductance (g_m) is fundamentally the rate of change of the drain current (I_{DS}) concerning the gate-to-source voltage (V_{GS}) around the chosen operating point. Mathematically, it's expressed as $g_m = \partial V_{GS} / \partial I_{DS}$.
- Utilize Square-Law Approximation for Analysis: To gain insight into g_m, you can fit the measured or simulated I_{DS} vs. V_{GS} data to a square-law equation. This comparison helps to assess whether the actual I_{DS} is changing more slowly or quickly than predicted by the ideal square-law model, indicating if g_m is underestimated or overestimated.

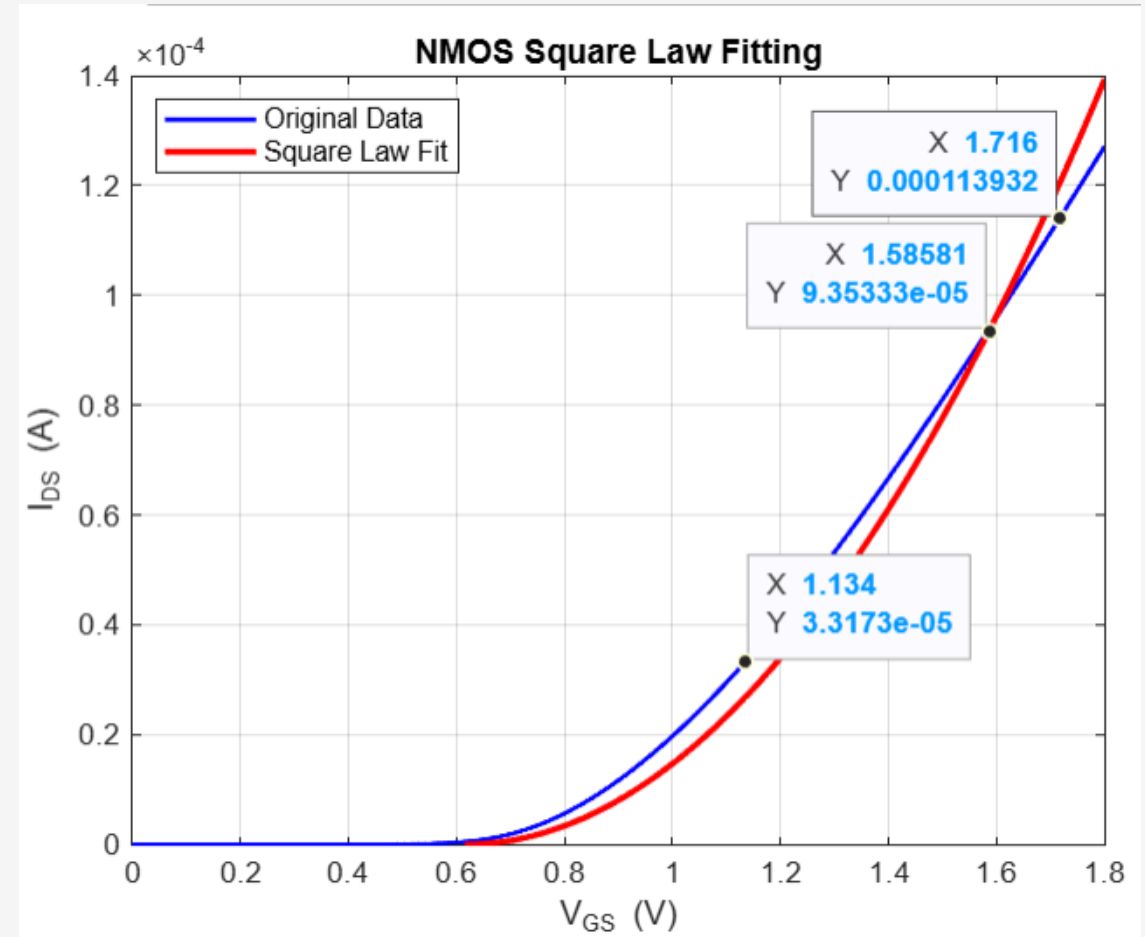


NMOS: Square Law Fitting (I_{ds} vs V_{gs})

 - Channel length of the NMOS is varied for an NMOS with width of 4 μ m and then the square law equation is fitted.
- Approximately the V_{th} is chosen (approximately chosen) and checked the R^2 value.




NMOS: Drain-to-Source Resistance

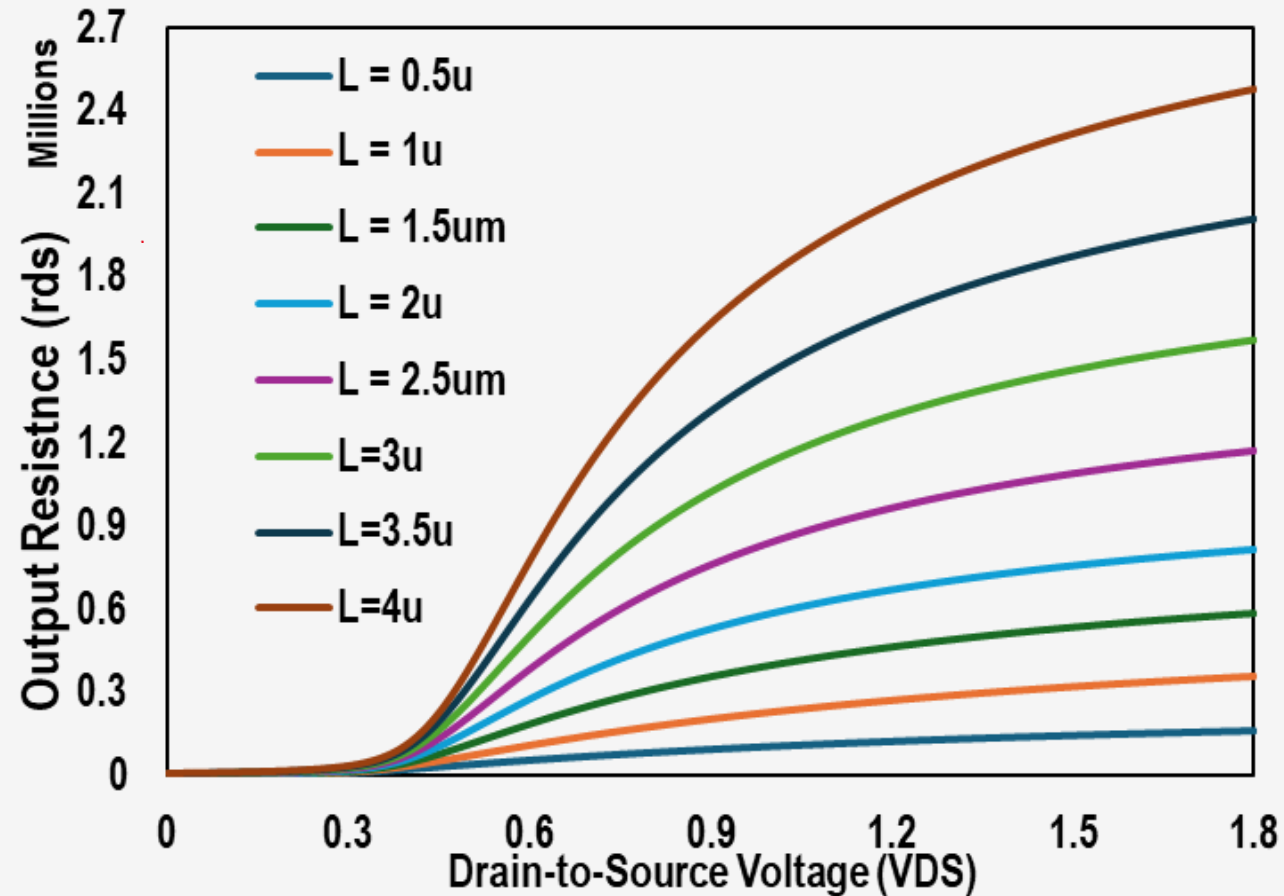- Channel length of the NMOS is varied for an NMOS with width of 4 μm .
- R_{ds} is plotted for various channel lengths.



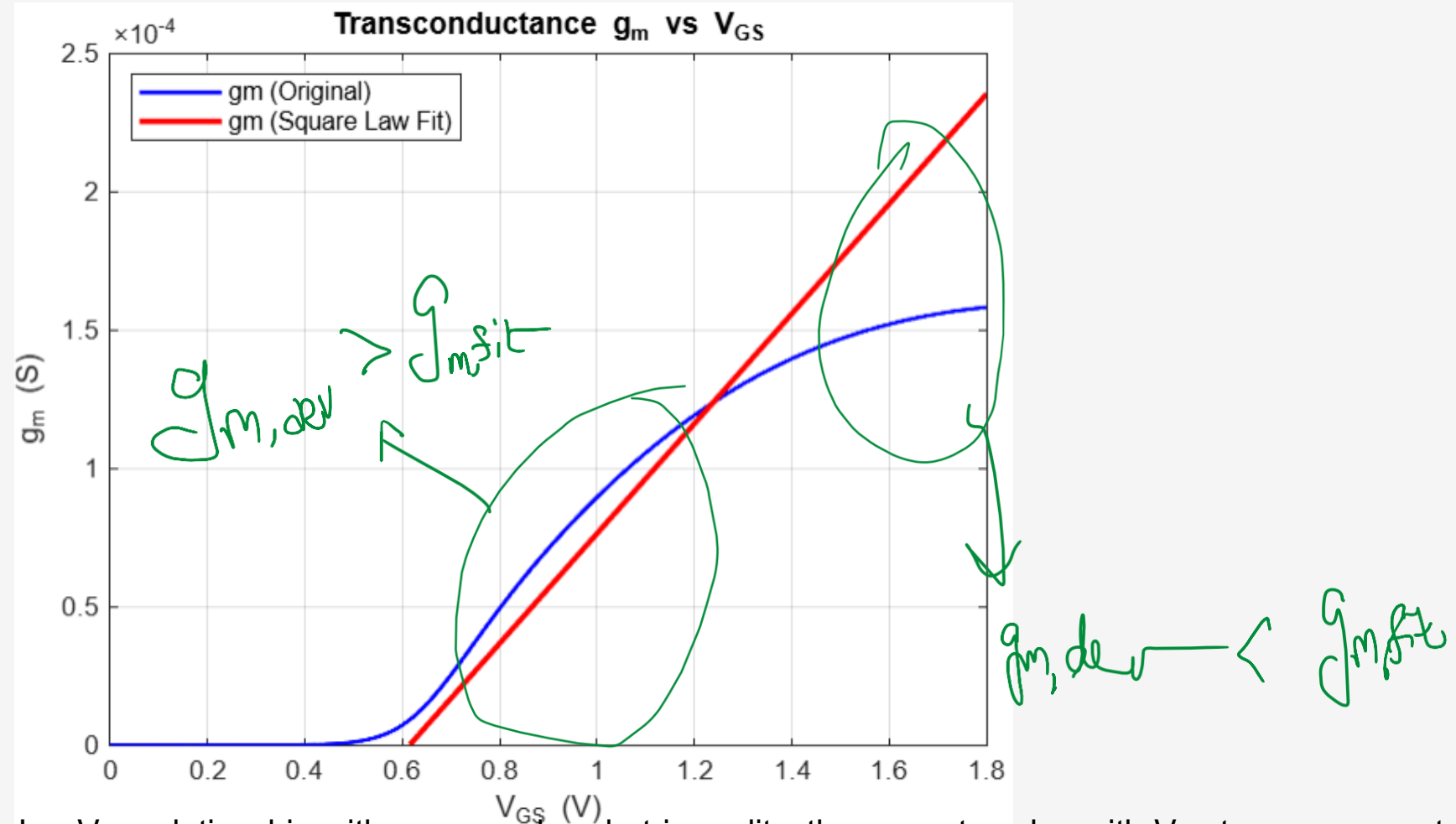
NMOS: W/L is (1 μ m/1 μ m) and V_{DS} is 1.8V and V_{GS} is varied from 0V to 1.8V



- We often approximate the I_{DS} - V_{GS} relationship with a square law, but in reality, the current scales with V_{GS} to an exponent typically ranging from 1 to 2. This non-ideal behavior means that relying on the simple square law equation will result in significant deviation in the calculated transconductance g_m .

Gm tracking with off-chip resistor and error understanding

- This circuit ensures that the transconductance (g_m) of transistor M_{n1} closely tracks the inverse of the off-chip resistor value (i.e., $g_{m_{n1}} \approx 1/R$), provided that the width-to-length (W/L) ratio of M_{n2} is scaled to be four times that of M_{n1} (i.e., $(W/L)_{mn2} = 4 \times (W/L)_{mn1}$).
- Assuming the off-chip resistance varies within a range from R_{min} to R_{max} , with a value R (where square-law equation holds), we analyze the impact on tracking accuracy. As the resistance R increases, the expected transconductance ($1/R$) decreases.
- However, due to nonidealities such as channel-length modulation, mismatch, and limited loop gain, the tracked $g_{m_{n1}}$ tends to overshoot, resulting in $g_{m_{n1}} > 1/R$.
- Conversely, when the off-chip resistance R decreases, the circuit attempts to track a higher target transconductance. In this case, the limitations in biasing and device operation may cause $g_{m_{n1}}$ to undershoot the ideal value, resulting in $g_{m_{n1}} < 1/R$.
- This deviation from ideal tracking becomes more significant toward the extremes of the resistor range and should be carefully considered in the design and calibration of g_m -based analog blocks.



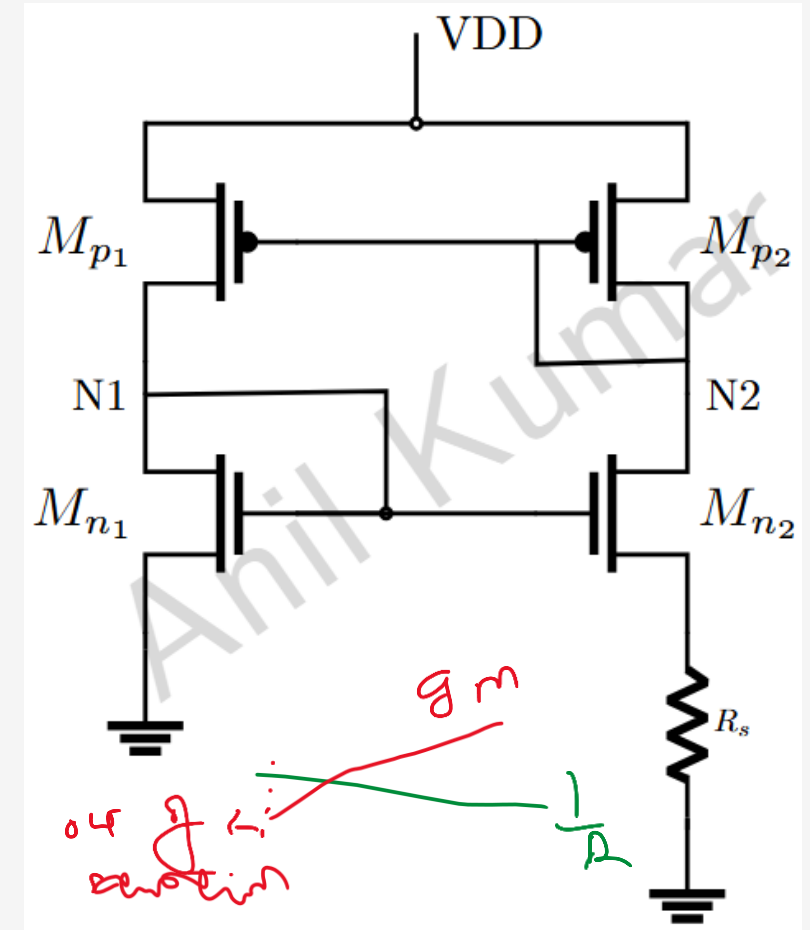


Gm tracking with off-chip resistor and error understanding

- While the beta-multiplier is designed to precisely control the transconductance (g_m) of a MOSFET (or one of the application) using an off-chip resistor, it is important to understand how precisely the transconductance of the device can be tracked with off-chip resistor.
- It's important to recognize that typical design analyses often assume the validity of the square-law equation for MOSFETs. However, this assumption does not hold true, even for devices with long channel length, due to various non-ideal effects.
- Hence it is very important to characterize and, at a minimum, qualitatively determine whether variations in the off-chip resistor lead to an underestimation or overestimation of the MOSFET's transconductance.

Gm tracking with off-chip resistor and error understanding


- Let us say, for a given sizing of the devices, transconductance (g_m) perfectly tracks the inverse of the off-chip resistor (R), meaning $g_m = 1/R$ and sets the operating point at 'A'.
- Here's how variations in the resistor R affect the operating point and transconductance:
- If the resistor R increases to $2R$:
 - Ideally, the current in device M_{n2} should halve and this current will be mirrored to M_{p1}
 - However, the operating point of M_{n1} shifts along the blue contour to 'C'.
 - This indicates that the actual g_m is higher than its expected value (which should be $1/(2R)$).
- Similarly, If the resistor R decreases to $R/2$. The operating point moves towards 'B'.
 - In this scenario, g_m decreases, or. the devices may even **move out of saturation**

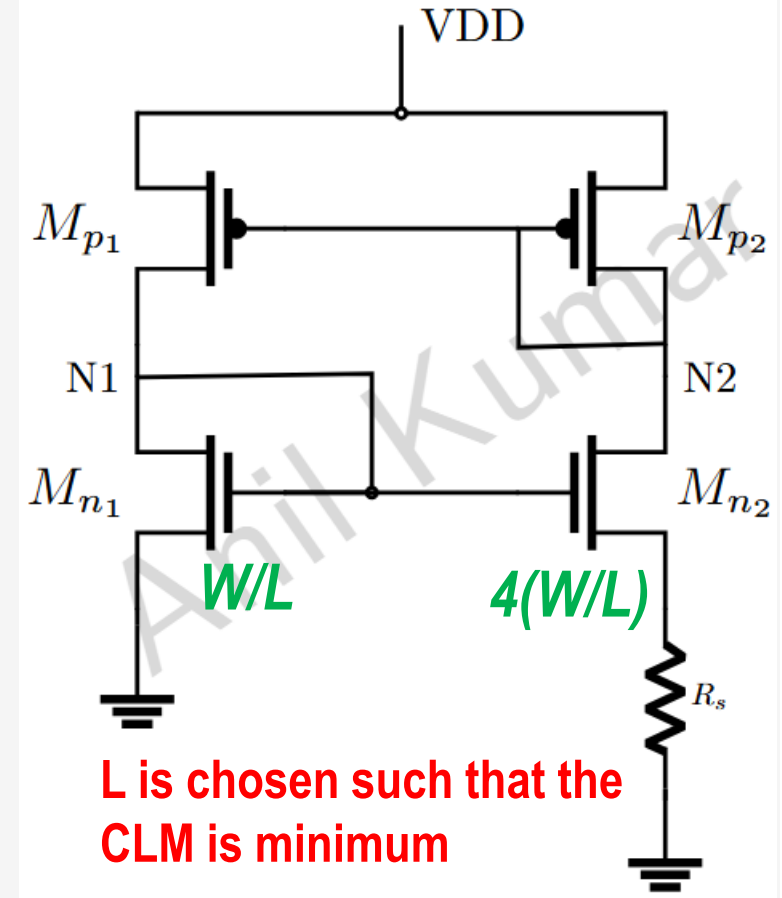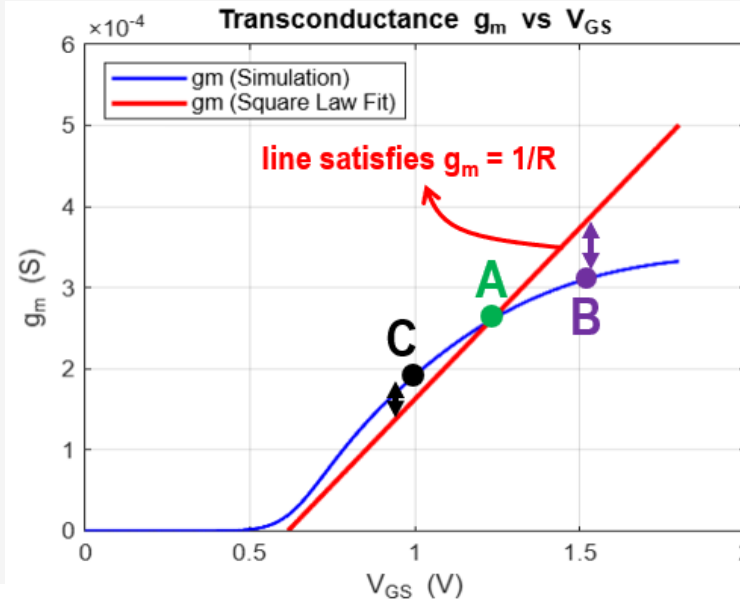 

Characterized using opensource skywater 130nm PDK

Ideas to develop

 - Finding the intersection point of both gm's after fitting the nearest square-law equation.
- If the device is biased to this current, it will hold all the square-law equations.
- Next step Next step (think)
- In this way, we can design the beta multiplier that exactly matches to off-chip resistor value



- We often approximate the $I_{DS}-V_{GS}$ relationship with a square law, but in reality, the current scales with V_{GS} to an exponent typically ranging from 1 to 2. This non-ideal behavior means that relying on the simple square law equation will result in significant deviation in the calculated transconductance g_m .

Sizing of the Beta - Multiplier

- $V_{DD} = 1.8V$. Choosing the appropriate PMOS and NMOS devices to allow better overdrive. In the SKY130A pdk, very little options of NMOS and PMOS devices are available.
- The lowest V_t of NMOS device apart from native and zero V_t is LVT device which is as high
- PMOS has nominal transistor flavor with $\sim 510mV$ and LVT flavor with as low as $\sim 280mV$
- Let's choose NMOS with LVT and PMOS with LVT flavors for the beta multiplier design

Device	Device	VDD (max)	Type	Threshold Voltage (mV)	V_{SG} (V)	V_{SD} (V)
nfet_01v8_lvt_nf	NMOS	1.8	Low V_t (with fingers)	570.48	1	1.8
pfet_01v8_lvt_nf	PMOS	1.8	Low V_t	282.5	1	1.8