

Tail Current Source Resistance in Common-Mode Gain of Diff. Amplifier

Dr. Anil Kumar Gundu





Role of Tail Current Source Resistance in Common-Mode Gain (I)

What is the impact of the tail current source's finite output resistance on the common-mode gain of a differential amplifier employing an active and perfectly matched current mirror if :

(i) the channel length modulation (CLM) of $M_1 - M_4$ are zero

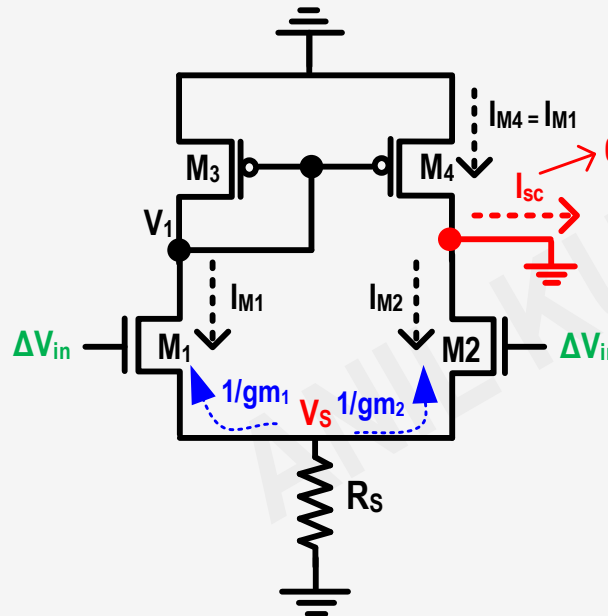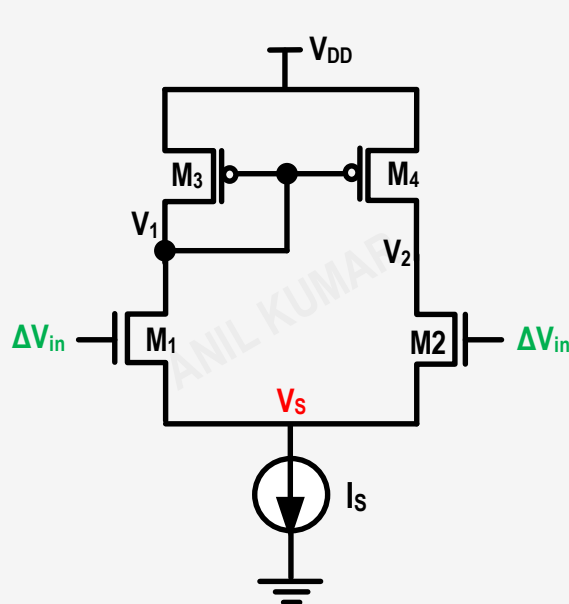(ii) The channel length modulation of M_1, M_2 is zero but the channel length modulation of transistors M_3 and M_4 is non-zero

Case (i) : The common-mode gain remains zero when the channel length modulation (CLM) of M_1, M_2, M_3 , and M_4 is zero, even with a finite output resistance in the tail current source. This is because identical currents through M_1 and M_2 result in a zero short-circuit current, as the current mirror (M_3-M_4) replicates this current. Thus, zero transconductance (G_m) leads to a zero common-mode gain.



$$I_{M1} = I_{M2} = \frac{g_m}{1+2g_m R_s} \Delta V_{in}$$

$$I_{M3} = \frac{g_m}{1+2g_m R_s} \Delta V_{in}$$

If M_3 and M_4 matched perfectly

$$I_{M4} = \frac{g_m}{1+2g_m R_s} \Delta V_{in}$$

$$I_{sc} = 0$$


Role of Tail Current Source Resistance in Common-Mode Gain (II)

What is the impact of the tail current source's finite output resistance on the common-mode gain of a differential amplifier employing an active and perfectly matched current mirror if :

(i) the channel length modulation (CLM) of M_1 , M_2 , M_3 , and M_4 are zero

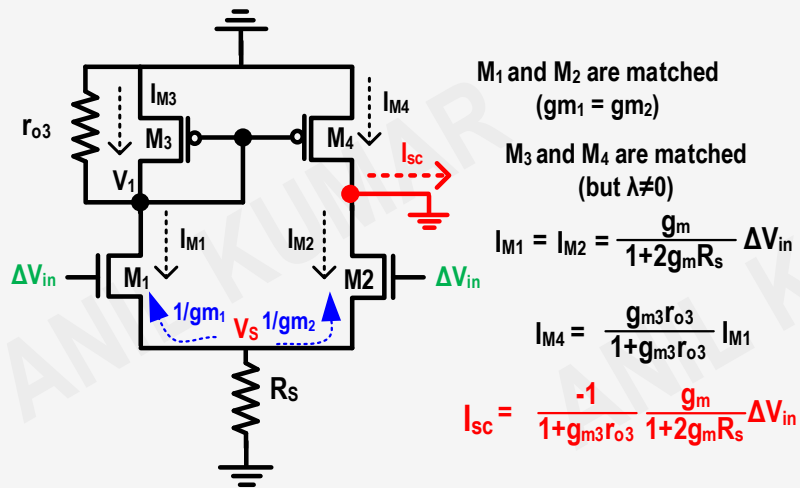(ii) The channel length modulation of M_1 , M_2 is zero but the channel length modulation of transistors M_3 and M_4 is non-zero

Case (ii) : I_{M1} splits between r_{o3} and $1/g_{m3}$. A fraction of current mirrored to M_4 and hence the structure exhibits transconductance. The output impedance looking into the output is r_{o4} (as CLM = 0 for M_1 and M_2) which eventually lead to a negative common-mode gain. To mitigate this, the transconductance multiplied by a source resistance ($2g_m R_s$) should be significantly larger than 1, implying that the sizing of input devices like M_1 and M_2 needs to be larger than that of the tail current source.



$$A_{CM} = \frac{-1}{1+g_{m3} r_{o3}} \frac{g_m r_{o4}}{1+2g_m R_s}$$

For lower common-mode gain,

$$2g_m R_s \gg 1$$

$$R_s \gg 1/2g_m$$

$$I_{M1} R_s \gg V_{od,M1}/4$$

$$V_s \gg \frac{V_{od,M1}}{2}$$

